

Roll No.

--	--	--	--	--	--	--	--	--	--

## SHAMBHUNATH INSTITUTE OF ENGINEERING AND TECHNOLOGY

Subject Code: BEC101

Subject: Fundamentals of Electronics Engineering

Course: B.Tech.

SEMESTER: I<sup>st</sup>

### SECOND SESSIONAL EXAMINATION, ODD SEMESTER, (2022-2023)

Branch: EC, CSE, EE, ME, CE

Time - 2 Hrs

Maximum Marks - 45

#### SECTION - A

1. Attempt all questions in brief.

Q N	QUESTION	Marks	CO	BL
a.	A 400 watt carrier is modulated to a depth of 75 percent. Calculate the total power in the modulated wave.	2	CO5	2
b.	Why BJT is called current controlled device?	2	CO2	2
c.	What is PIV for half-wave and full-wave centre-tapped transformer rectifier?	2	CO1	3
d.	State two differences between FET and BJT.	2	CO2	1
e.	What is the need for modulation?	2	CO5	1
f.	Draw the V-I characteristics of an ideal diode in forward and reverse bias conditions.	2	CO1	6

#### SECTION - B

2. Attempt any ONE part of the following :

Q N	QUESTION	Marks	CO	BL
a.	Draw and explain the working of a bridge rectifier with input and output waveforms. Calculate efficiency and ripple factor.	5	CO1	5
b.	Draw the block diagram of a communication system and explain each block in brief.	5	CO5	6

3. Attempt any ONE part of the following:

Q N	QUESTION	Marks	CO	BL
a.	What is voltage multiplier? Draw and explain the voltage doubler circuit.	5	CO1	3
b.	Describe the construction and working of a NPN transistor in CE configuration with respect to size and doping.	5	CO2	6

4. Attempt any ONE part of the following:


	QUESTION	Marks	CO	BL
a.	Describe working of n-channel JFET with help of constructional diagram and draw its drain and transfer characteristics.	5	CO2	4
b.	Explain the input and output characteristics of a BJT in the CE configuration.	5	CO5	1

### SECTION - C

5. Attempt any ONE part of the following:

Q N	QUESTION	Marks	CO	BL
a.	Explain the V-I characteristics of PN junction diode.	6	CO1	2
b.	For a JFET given $I_{DSS} = 6 \text{ mA}$ and $V_P = -4.5 \text{ V}$ : a. Determine $I_D$ at $V_{GS} = -2 \text{ V}$ and $-3.6 \text{ V}$ . b. Determine $V_{GS}$ at $I_D = 3 \text{ mA}$ and $5.5 \text{ mA}$ .	6	CO2	1

6. Attempt any ONE part of the following:

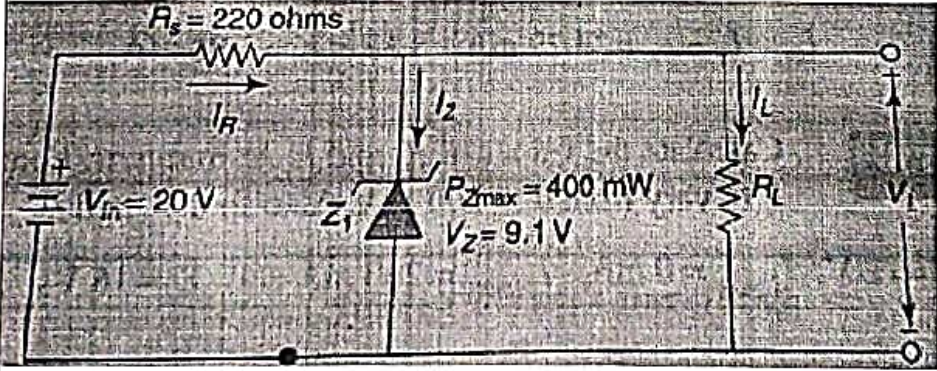Q N	QUESTION	Marks	CO	BL
a.	(i) Prove the following relation between total power and carrier power in AM wave. $P_t = P_c \left(1 + \frac{m^2}{2}\right)$ (ii) The antenna current of an AM transmitter is 8 ampere when only the carrier is sent, but it increases to 8.93 ampere when the carrier is modulated by a single sine wave. Find the percentage modulation. Determine the antenna current when the percent of modulation changes to 0.8.	6	CO5	3
b.	Determine $V_L$ , $I_R$ , $I_L$ , $I_Z$ for the given circuit. $R_i$ is $470\Omega$ . 	6	CO1	5

7. Attempt any ONE part of the following:

Q N	QUESTION	Marks	CO	BL
a.	Write short notes on (a) LED (b) Tunnel Diode	6	CO1	1
b.	Define Amplitude Modulation. Derive the expression for AM modulated waveform.	6	CO5	2



Roll No.

22BTCS0260

**SHAMBHUNATH INSTITUTE OF ENGINEERING AND TECHNOLOGY**

Subject Code: BEC 101

Subject: Fundamentals of Electronics Engineering

Course: B.Tech.

SEMESTER: 1<sup>st</sup>

FIRST SESSIONAL EXAMINATION, ODD SEMESTER, (2022-2023)

Branch: (CE/EC/EE/ME/CS)

Time -1hr 30 min

Maximum Marks - 30

NOTE: Attempt all sections

**SECTION - A**

1. Attempt all questions in brief.

(4\*2 = 8)

Q N	QUESTION	Marks	CO	BL
a.	Define the terms: (i) Minterm (ii) Maxterm	2	4	L1
b.	Write the characteristics of an ideal op-amp.	2	3	L1
c.	For a given op-amp, CMRR=10 <sup>4</sup> and A <sub>v</sub> =10 <sup>5</sup> , find its common mode gain.	2	3	L3
d.	Simplify the Boolean function using Boolean Algebra theorems: $A'B'C' + A'B'C + A'B'C' + A'B'C'$	2	4	L5

**SECTION - B**

2. Attempt any ONE part of the following:

(1\*5 = 5)

Q N	QUESTION	Marks	CO	BL
a.	Draw the circuit diagram of noninverting amplifier using op-amp; derive the expression for voltage gain.	5	3	L5
b.	Simplify the following logical expression using K-map $Y(A,B,C,D) = \sum m(1,3,4,6,8,9,11,13,15) + d(0,2,14)$ . Realize the minimized expression using the basic gates.	5	4	L5

**SECTION - C**

3. Attempt any ONE part of the following:

(1\*5 = 5)

Q N	QUESTION	Marks	CO	BL
a.	Write technical short notes on the following: (i) Inverting comparator (ii) Differential and Common-Mode Operation	5	3	L1
b.	Minimize using K-map and realize using basic gates only. $F(A, B, C, D) = \prod M(3, 4, 5, 7, 9, 13, 14, 15). d(0, 2, 8)$ .	5	4	L3

4. Attempt any ONE part of the following:

(1\*6 = 6)

Q N	QUESTION	Marks	CO	BL
a.	Explain how the basic gates can be realized using NAND gates only.	6	4	L2
b.	Draw a differential amplifier circuit using op-amp and find the output voltage in terms of different input voltage.	6	3	L5

5. Attempt any ONE part of the following:

(1\*6 = 6)

Q N	QUESTION	Marks	CO	BL
a.	Convert the following :- i) $(1101.00101)_2 = ( )_{10}$ ii) $(457)_{10} = ( )_{16}$ iii) $(101110.0101)_2 = ( )_{10}$ iv) $(82.35)_{10} = ( )_{16}$ v) $(ABC.75)_{16} = ( )_{10}$	6	4	L5
b.	Draw the circuit diagram of integrator and differentiator using op-amps, derive the expression its output voltage.	6	3	L5