

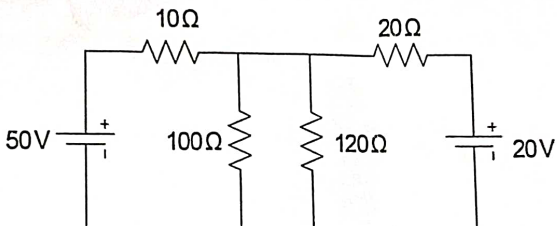
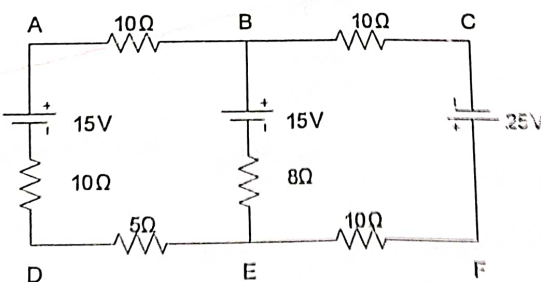
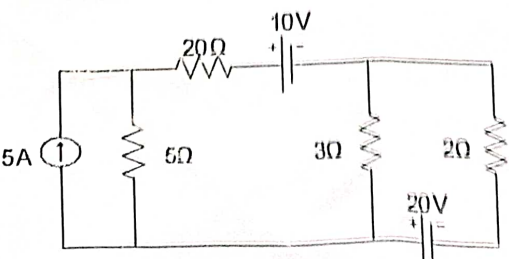
SECTION – A

1. Attempt all questions in brief.

Q N	QUESTION	Marks	CO	BL
a.	Explain the following. (i) Active and passive element (ii) Unilateral and bilateral elements.	2	CO1	L2
b.	State and explain Kirchhoff's voltage law.	2	CO1	L2
c.	State and explain Kirchhoff's current law.	2	CO1	L2
d.	Distinguish between ideal and practical voltage source. Also draw their VI characteristics.	2	CO1	L1

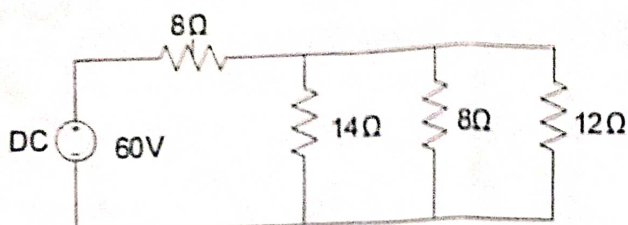
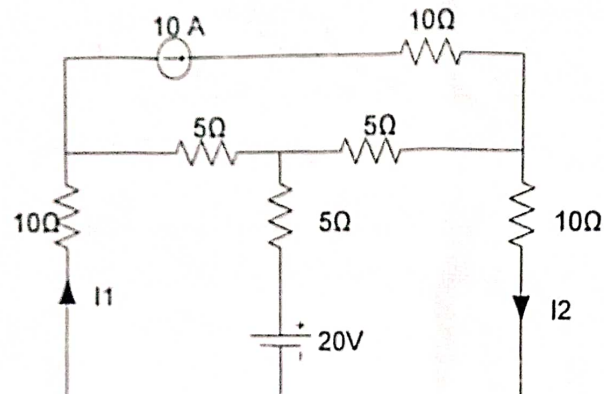
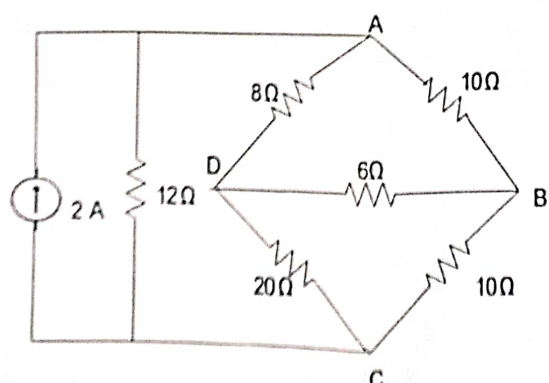
SECTION - B

2. Attempt any TWO parts of the following.

Q N	QUESTION	Marks	CO	BL
a.	<p>Using nodal method, find current through $100\ \Omega$ resistor.</p> 	5	CO1	L3
b.	<p>Find the current in the $8\ \Omega$ resistor in the circuit using loop (mesh) analysis method.</p> 	5	CO1	L3
c.	<p>Find the current in, and voltage across the $2\ \Omega$ resistance in the following figure.</p> 	5	CO1	L3

SECTION - C

3. Attempt any TWO parts of the following:

Q N	QUESTION	Marks	CO	BL
a.	<p>In the network, find the power delivered by the source using the nodal analysis.</p> 	6	CO1	L3
b.	<p>Using mesh analysis, calculate the currents I_1 and I_2.</p> 	6	CO1	L3
c.	<p>Using mesh current method, find the currents in resistances $10\ \Omega$, $6\ \Omega$, $20\ \Omega$ and $10\ \Omega$ in the circuit.</p> 	6	CO1	L3

Bloom's Taxonomy Level (BL):-

Remember (L1),

Understanding (L2),

Apply (L3),

Analyze (L4),

Evaluating (L5),

Creating (L6)